

# Electronic and Microcontroller



# Analog or Digital ?

Analog: continuously valued signal with infinite possible values, such as temperature

Digital: discretely valued signal, such as integers encoded in binary

Discussion about electric current

$$1,609 \cdot 10^{-19} \text{C}$$
$$I = Q / t$$

$$U = 3,5 \text{V}$$
$$= 3,5178347$$

$$\frac{P \text{ V}}$$

# DAC – Transfer Characteristics

- > Binary numbers need to be converted to analog voltage.
- > Example 8-Bit number (0-255) to voltage (0-2,55V)  
1-Bit (LSB)  $\Leftrightarrow$  0,01V

$$\Delta T = -40^{\circ}\text{C} \dots +60^{\circ}\text{C}$$

$$100^{\circ}\text{C} \dots 200 \times 0,5^{\circ}$$

Temp  $\rightarrow$  8-Bit


# DAC – Time-varying voltage

a) Array → Werte im Speicher  
 b) CPU → Wert berechnen

> Table with values for every timeslice. ( $1 \cdot \sin(t)$ )

Vout	t
0	0
0,5	30
0,71	45
0,87	60
1	90
0,87	120
0,71	135

0,5                      150


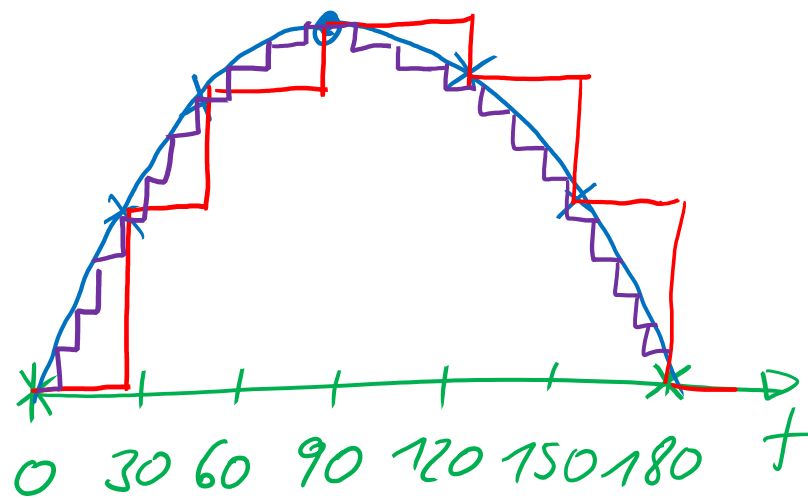


**DMA**
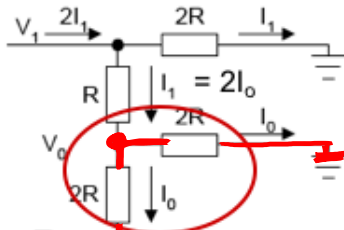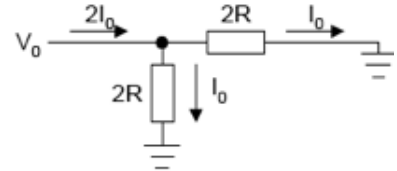
# DAC – R-2R Ladder

We want to generate currents  $I_0, 2I_0, 4I_0, \dots$

- ◆ Two  $2R$  resistors in parallel means that the  $2I_0$  current will split equally and equivalent resistance  $R$



- ◆ The Thévenin resistances of the two branches at  $V_1$  both equal  $2R$  so the current into this node will split evenly

- We already know that the current into node  $V_0$  is  $2I_0$ , so it follows that  $I_1 = 2I_0$



$= R$

- ◆ We can repeat this process indefinitely and, using only two resistor values, can generate a whole series of currents where  $I_n = 2^n I_0$

From the voltage drop across the horizontal resistors, we see that  $V_n = 2RI_n = 2^{n+1}RI_0$

- For an  $N$ -bit ladder the input voltage is therefore
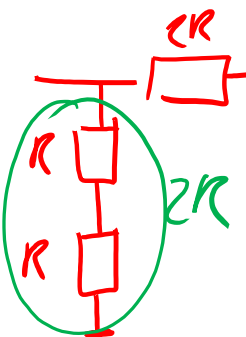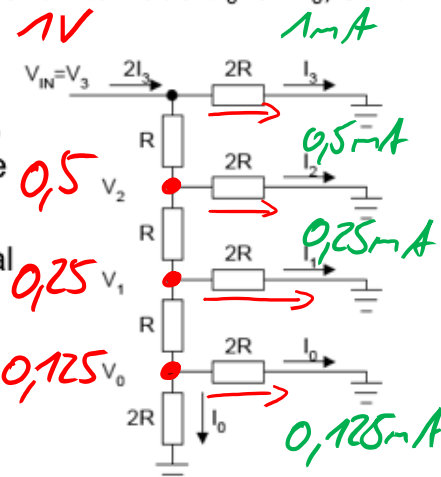
$$V_{in} = 2^N RI_0 \Rightarrow I_0 = 2^{-N} V_{in} / R$$



> Picture from [http://www.ee.ic.ac.uk/pcheung/teaching/ee2\\_digital/Lecture%209%20-%20Digital-to-Analogue%20Conversion.pdf](http://www.ee.ic.ac.uk/pcheung/teaching/ee2_digital/Lecture%209%20-%20Digital-to-Analogue%20Conversion.pdf)

# DAC – Current Switched DAC

- ◆ Total current into summing junction is  $X_{3:0} \times I_0$

- Hence  $V_{out} = X_{3:0} \times V_{in} / 16R \times -R_f$

- ◆ We switch currents rather than voltages so that all nodes in the circuit remain at a constant voltage

⇒ no need to charge/discharge node capacitances


⇒ faster

- ◆ Use CMOS transmission gates as switches: adjust ladder resistors to account for switch resistance

- Each 2-way switch needs four transistors

- ◆ As required by R/2R ladder, all the switch output terminals are at 0 V.

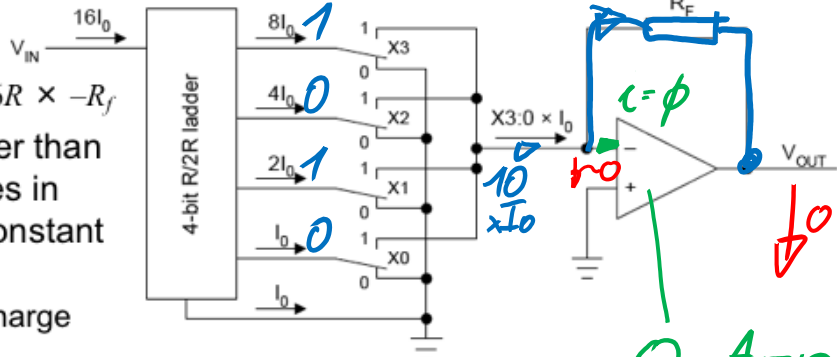- ladder outputs are always connected either to ground or to a virtual earth



> Picture from [http://www.ee.ic.ac.uk/pcheung/teaching/ee2\\_digital/Lecture%209%20-%20Digital-to-Analogue%20Conversion.pdf](http://www.ee.ic.ac.uk/pcheung/teaching/ee2_digital/Lecture%209%20-%20Digital-to-Analogue%20Conversion.pdf)

# DAC – STM32 - mbed


```
#include "mbed.h"

// The sinewave is created on this pin
AnalogOut aout(PA_4);

int main()
{
    const double amplitude = 1000;
    const double offset = 16000;
    uint16_t sample = 0;


    while(1) {
        // ramp output
        for (int i = 0; i < 16; ++i) {
            sample = (uint16_t)(amplitude * i + offset);
            aout.write_u16(sample);
            wait_ms(5);
        }
    }
}
```

L476

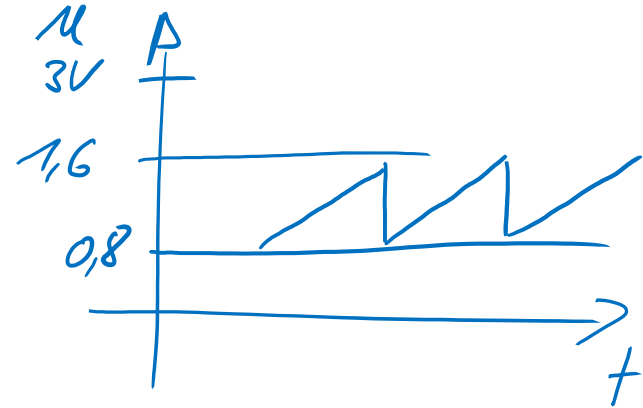

# DAC – STM32 - LEO

## Connect L476-A2 with F303-A3

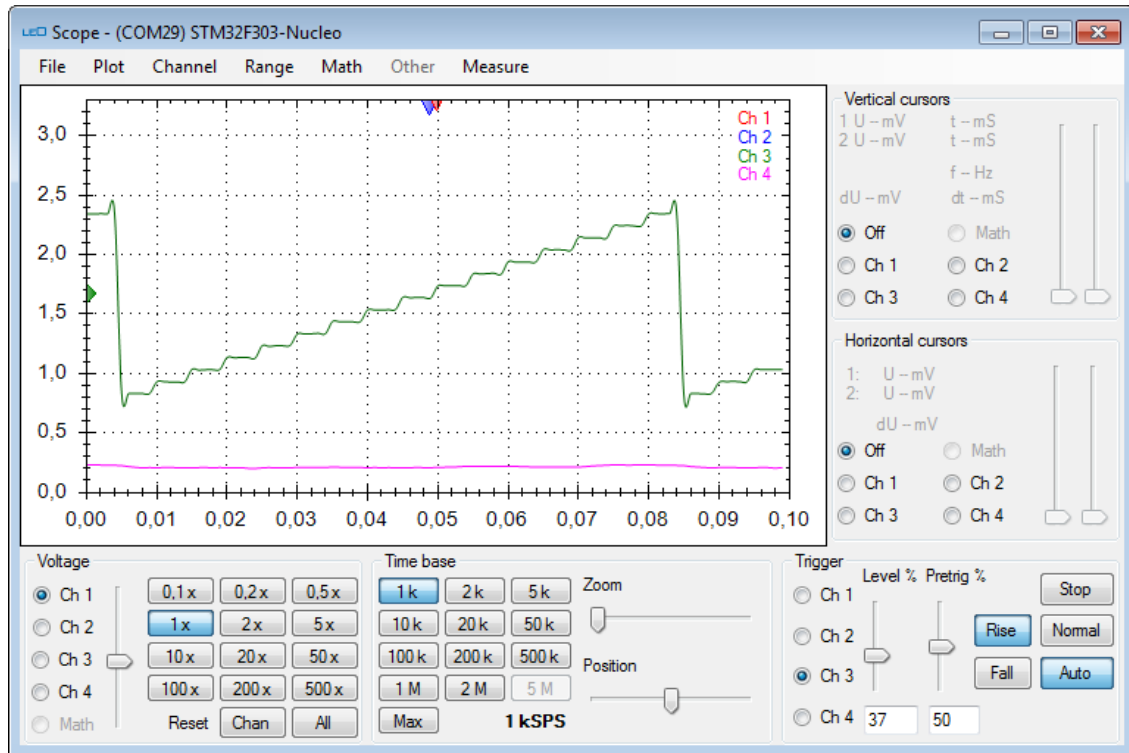



# DAC – STM32 - mbed

```
#include "mbed.h"


// The sinewave is created on this pin
AnalogOut aout(PA_4);

int main()
{
    const double amplitude = 10;
    const double offset = 16000;
    uint16_t sample = 0;

    while(1) {
        // ramp output
        for (int i = 1; i < 1600; i++) {
            sample = (uint16_t)(amplitude * i + offset);
            aout.write_u16(sample);
            wait_ms(0.1);
        }
    }
}
```

# DAC – STM32 - LEO

## Connect L476-A2 with F303-A3

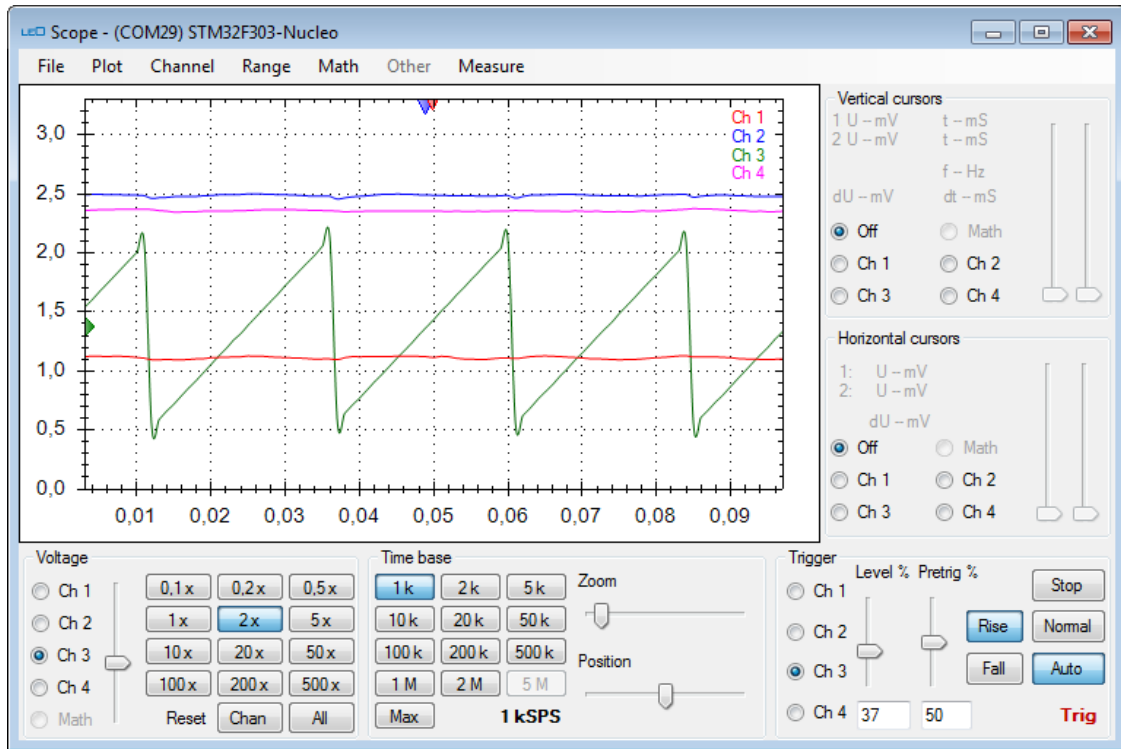

# DAC – STM32 - mbed

```
#include "mbed.h"


// The sinewave is created on this pin
AnalogOut aout(PA_4);

int main()
{
    const double pi = 3.141592653589793238462;
    const double amplitude = 0.5f;
    const double offset = 65535/2;
    double rads = 0.0;
    uint16_t sample = 0;

    while(1) {
        // sinewave output
        for (int i = 0; i < 360; i++) {
            rads = (pi * i) / 180.0f;
            sample = (uint16_t)(amplitude * (offset * (cos(rads + pi)))) + offset);
            aout.write_u16(sample);
            wait_ms(0.1);
        }
    }
}
```

# DAC – STM32 - LEO

## Connect L476-A2 with F303-A3

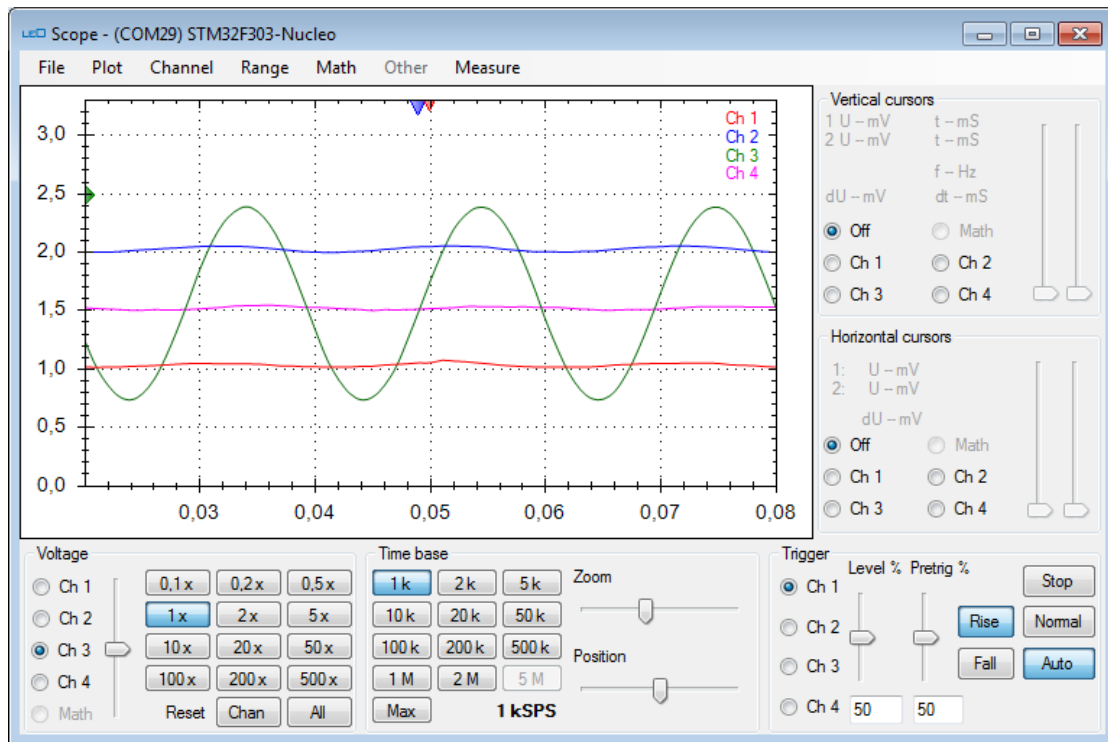



**Analog Voltage  
OUT**